



# USB Receiver Unit


- Two-week, individual lab
- Three phases
  - Diagrams, code and sub-block test benches (start of lab, Feb 24-26)
  - Submit source and top-level test bench (11:59 PM, March 1-3)
  - Submit mapped version (start of lab, March 3-5)




# Project

- Think of a design that is applicable for an ASIC (or a FPGA). A microcontroller should not be adequate due to high speed/low power requirements (NO ELEVATOR CONTROLLERS)
- Think about a parallel design
- Blackboard contains past project ideas. Good ideas include protocol interfacing and signal processing... (no math co-processors)
- Due to time limitations, a subset of a given protocol may be acceptable
- Work in groups of 3-4 ONLY IN YOUR SECTION
- See Project Idea Guidelines posted online (due next week), you are encouraged to submit multiple ideas.

# Simplified USB Interface

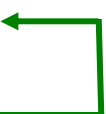- Read-only USB interface, subset of USB 1.1
  - Recognizes USB data packets
  - Puts data into a FIFO
  - Higher level functions handled by external controller (CRC decode, addressing protocol etc.)
- Differential input lines D+, D-
- NRZi (inverted Non Return to Zero) encoding
  - requires synchronous edge detection
- Sync (start) byte how well would this work for UART? 
- Clock synchronization (using data transitions)
- Real USB includes “bit-stuffing” (we won’t)
  - used to ensure that clock is resynchronized often enough
- End of packet signal –  $D+ = D- = 0$
- Data written to FIFO Queue for interface to external device (provided)

# NRZi encoding/decoding

 

<u>Original Data</u>		<u>Encoded data</u>
0	=>	0->1 or 1->0 transition
1	=>	no transition


To decode: have to compare current and previous bit.  
If same, data = 1. If different, data = 0.

What logic gate has similar behavior?

- a. NAND
- b. XOR
- c. XNOR
- d. INV
 
# NRZi encoding/decoding

Note – the output of an actual encoder or decoder will be delayed by one bit period.




<u>Original Data</u>		<u>Encoded data</u>
0	=>	0->1 or 1->0 transition
1	=>	<b>no transition</b>

To decode: have to compare current and previous bit.  
If same, data = 1. If different, data = 0.


What logic gate has similar behavior?

- a. NAND
- b. XOR
- c. XNOR
- d. INV

# Sync Byte (encoded)

 


SYNC  
pattern  
on USB  
bus

 

Which bits of  
the incoming  
waveform were  
decoded to  
produce the  
MSB in the shift  
register? the  
LSB?

# End of Packet (EOP) Signal

 

USB uses two data lines


- normally one is the complement of the other
- eliminates common mode noise

Both data lines are pulled low to signal EOP


Can be detected by a single logic gate

# Complete Packets

- Begins with SYNC byte

 

 
- Packet body is decoded and stored in FIFO, one byte at a time
- Ends with EOP signal








# System Overview

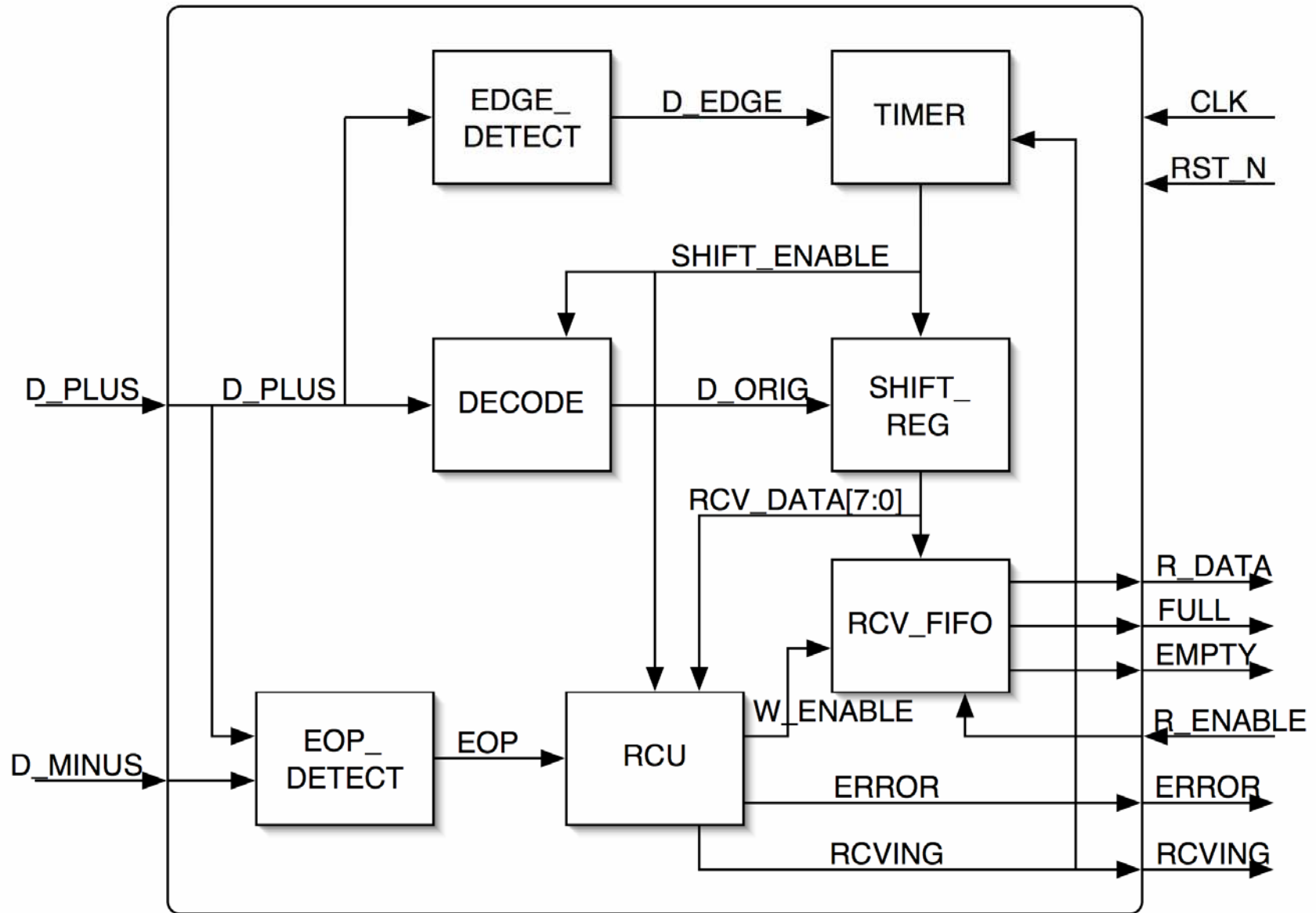

# Synchronous Edge Detection

 

Hint: this is useful for NRZi decoding and for clock sync.

Depending on choice of logic gate, this will generate a one clock cycle pulse for:


- input rising transition
- input fall transition
- either a rising or falling transition
- if there is no transition

Thought question: is this circuit suitable as a synchronizer?

This assumes system clock period is shorter than time between input data transitions

# DECODE

- Reverses NRZI encoding

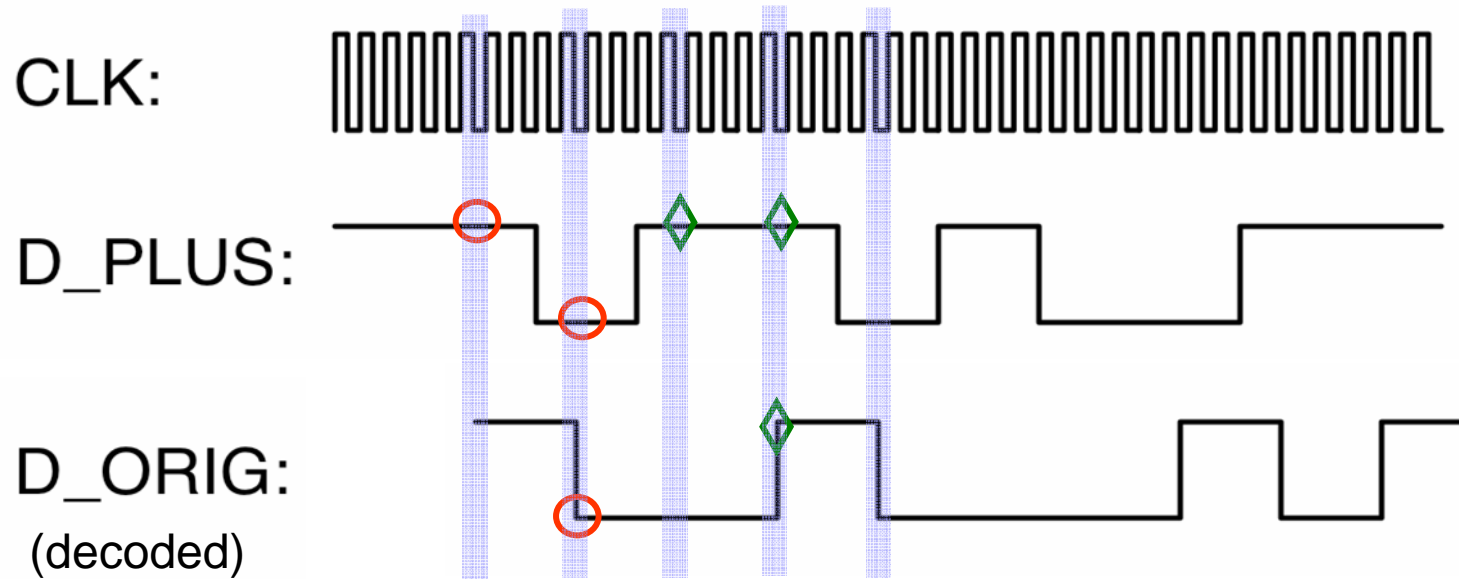


the shapes indicate examples of the correspondence between the NRZI input and the decoded output

the vertical bars indicate shift strobes which cause input data to shift to the right by one position in the decoder flip-flops
 
# EDGE\_DETECT




- Detects transitions on the D\_PLUS input
- Synchronizes TIMER block




note that edge detect pulse may be delayed by one clock cycle



# TIMER

 


- Shifts next bit every 8 clock cycles

 

 
# SHIFT\_REG



- Shifts data in on each clock cycle when SHIFT\_ENABLE is asserted.
- 3-bit shift register illustrated below, actual is 8 bit.



# RCV\_FIFO

 


- The FIFO is **provided**, “wrapper” file.
- FIFO writes data from RCV\_DATA when W\_ENABLE is high on a clock edge.
- FIFO outputs data on R\_DATA, increments to next byte when R\_ENABLE is high.
- FULL and EMPTY indicate FIFO status
- Provided FIFO has two clocks
  - Why? This FIFO was designed to provided interface between circuits running on different clocks
  - you will tie them to same system clock
 
# EOP\_DETECT




- High when D\_PLUS and D\_MINUS are both low.
- Ridiculously easy





# RCU

 

- Controls USB Receiver circuit
- Begins receiving when an edge is detected.
- Checks to see if the SYNC byte was received, error condition if not.
- Stop receiving when the EOP is detected.


# Sequence of Operation

- On reset, the RCU goes to the idle (waiting) state.
- When an edge is first detected,
  - begin receiving data through the DECODE block to the SHIFT\_REG.
  - Set the RCVING line high.
- After the first byte is shifted in
  - check that byte matches USB SYNC byte.
  - If byte matches SYNC, do not store to FIFO, but begin receiving and storing data from next byte.
  - If the byte does *not* match the SYNC byte,
    - set R\_ERROR flag to 1
    - disregard any input until the next EOP is reached.
    - RCVING line should remain high until the EOP is reached.
    - R\_ERROR flag should remain high until the next packet begins.
- Continue receiving and storing data to FIFO until the EOP is detected, then set the RCVING line low.
- If an EOP is reached with an incomplete byte in the shift register
  - set the ERROR flag high and do not store the last byte.
  - Leave the R\_ERROR flag high until the next packet begins.



# FIFO RAM

# FIFO Design (provided)

 

Why can't this be done with a simple shift register?


## ■ Purpose:

- Efficiently handle data transfer between two systems
- Allows source & receiver of data to operate at different speeds (& clock rates)

## ■ Some Requirements:


- Data must be read out in same order as written in
- **Can't assume synchronization between input and output**
- **Next word in FIFO must be immediately available to read.**

# FIFO Operation

 


Prior to writing anything  
FIFO is empty, Write Ptr = Read Ptr

# FIFO Operation

 


After 1<sup>st</sup> word written

# FIFO Operation

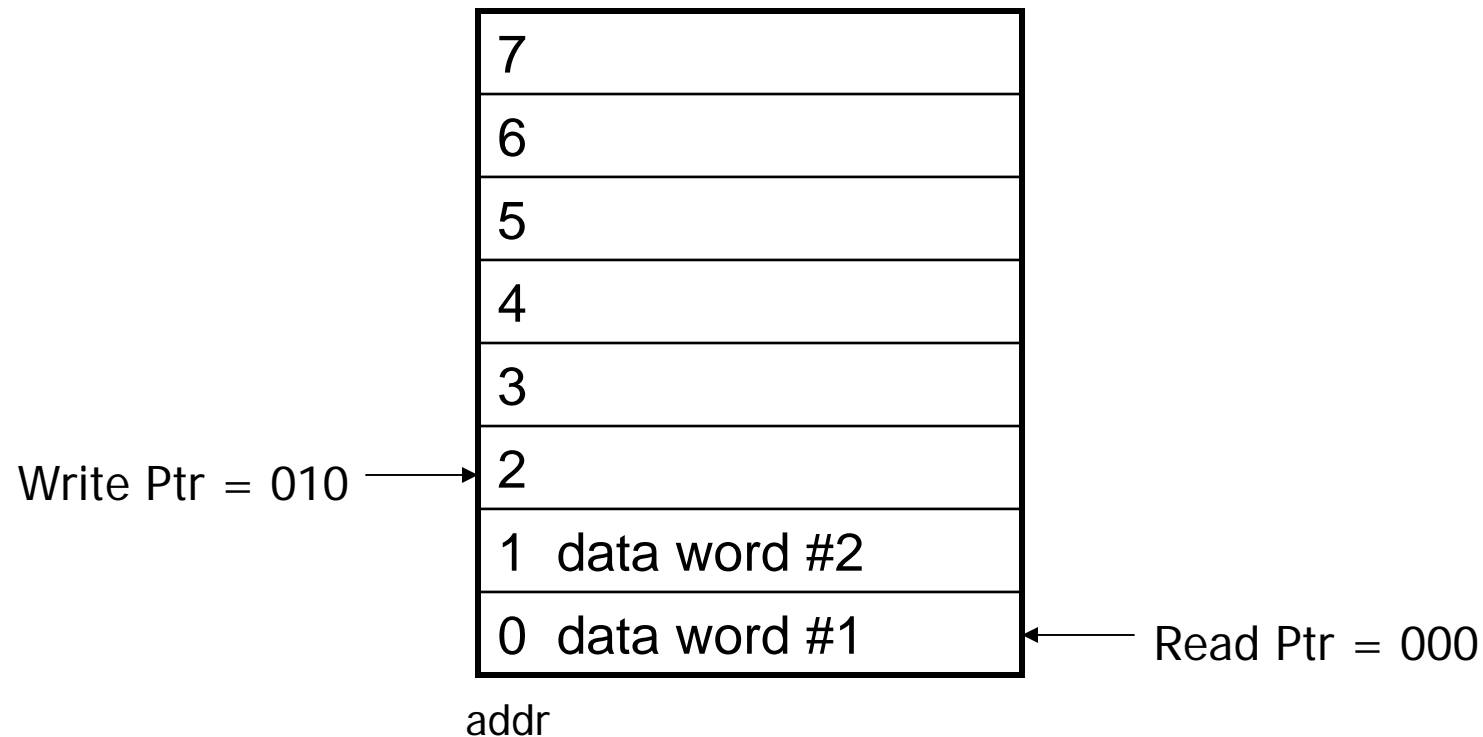

After 2<sup>nd</sup> word written


# FIFO Operation

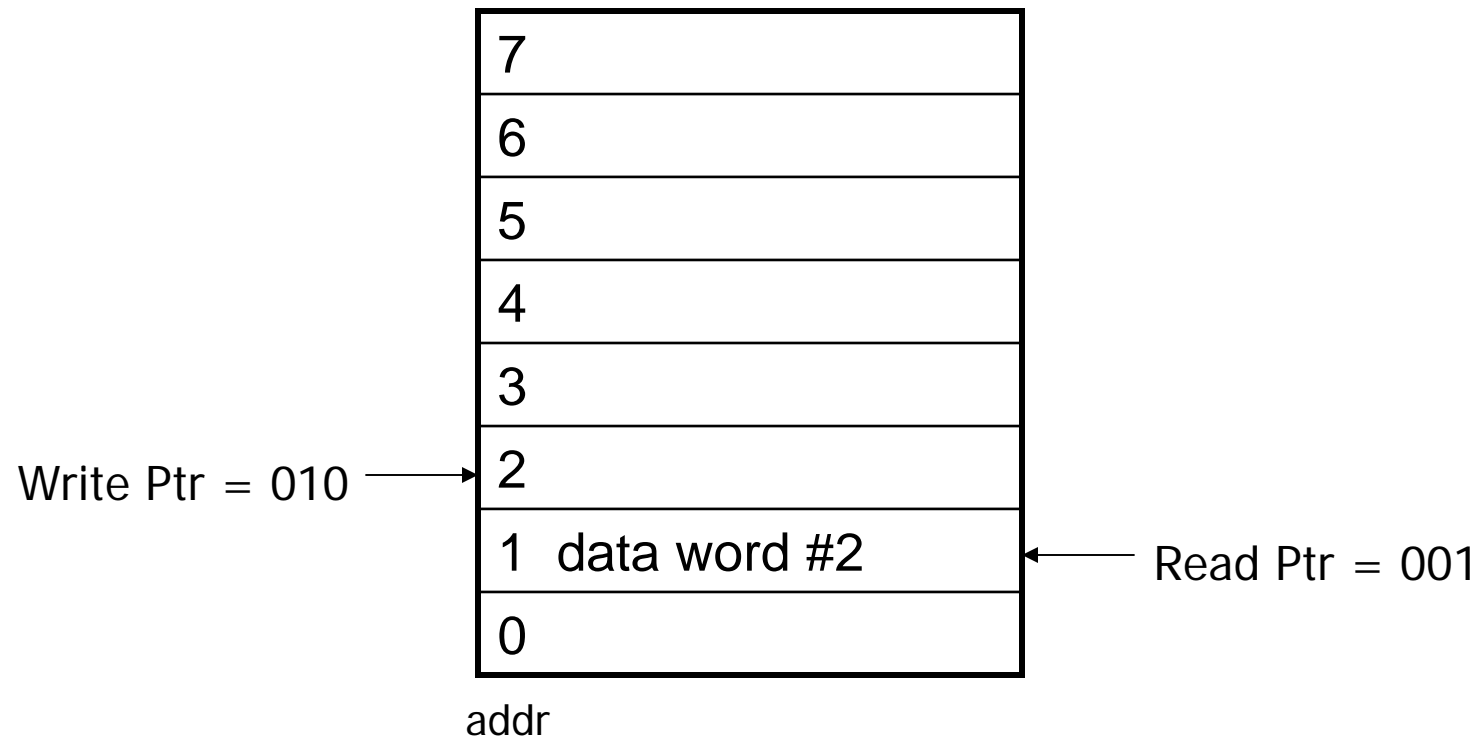

After 1<sup>st</sup> word read




# FIFO Operation

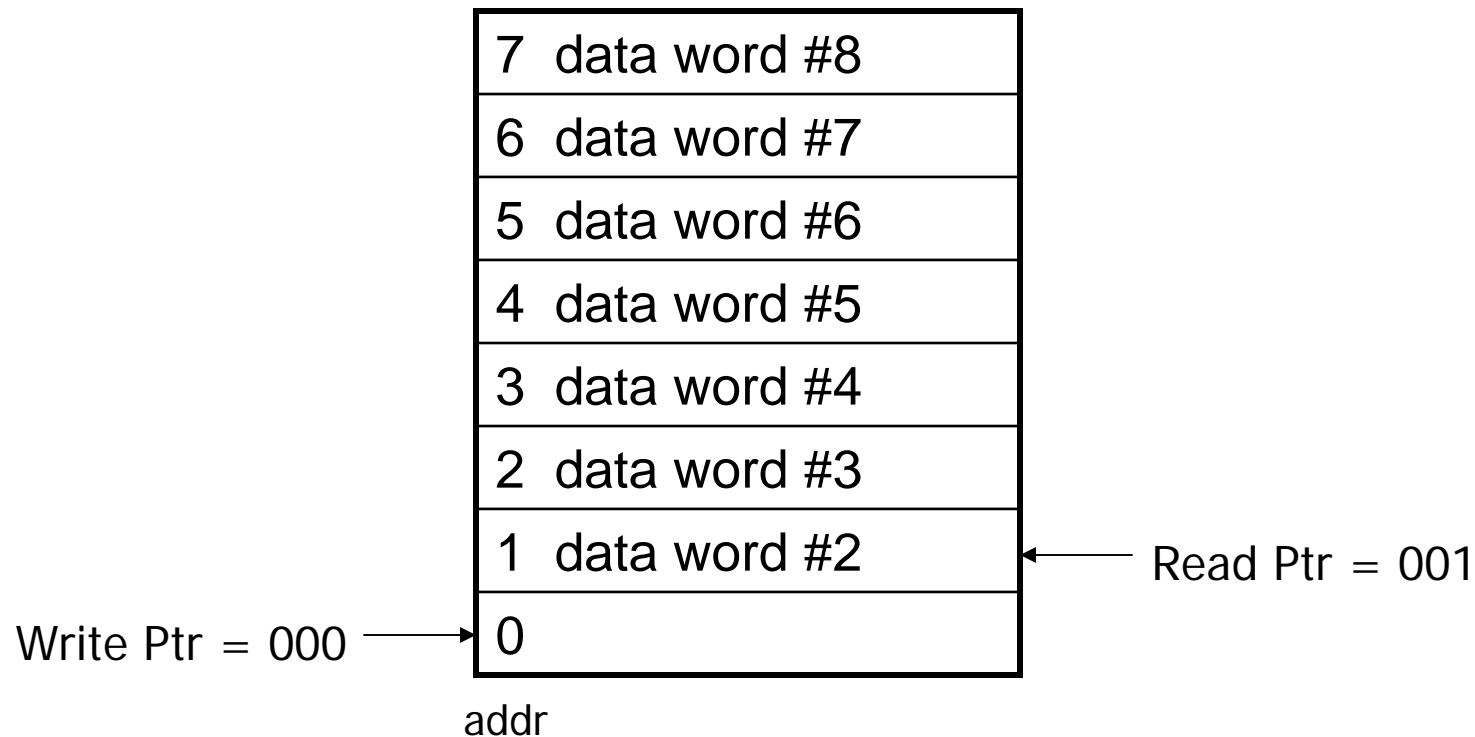


After 7 more words written  
Notice write pointer wrapped around

# FIFO Operation

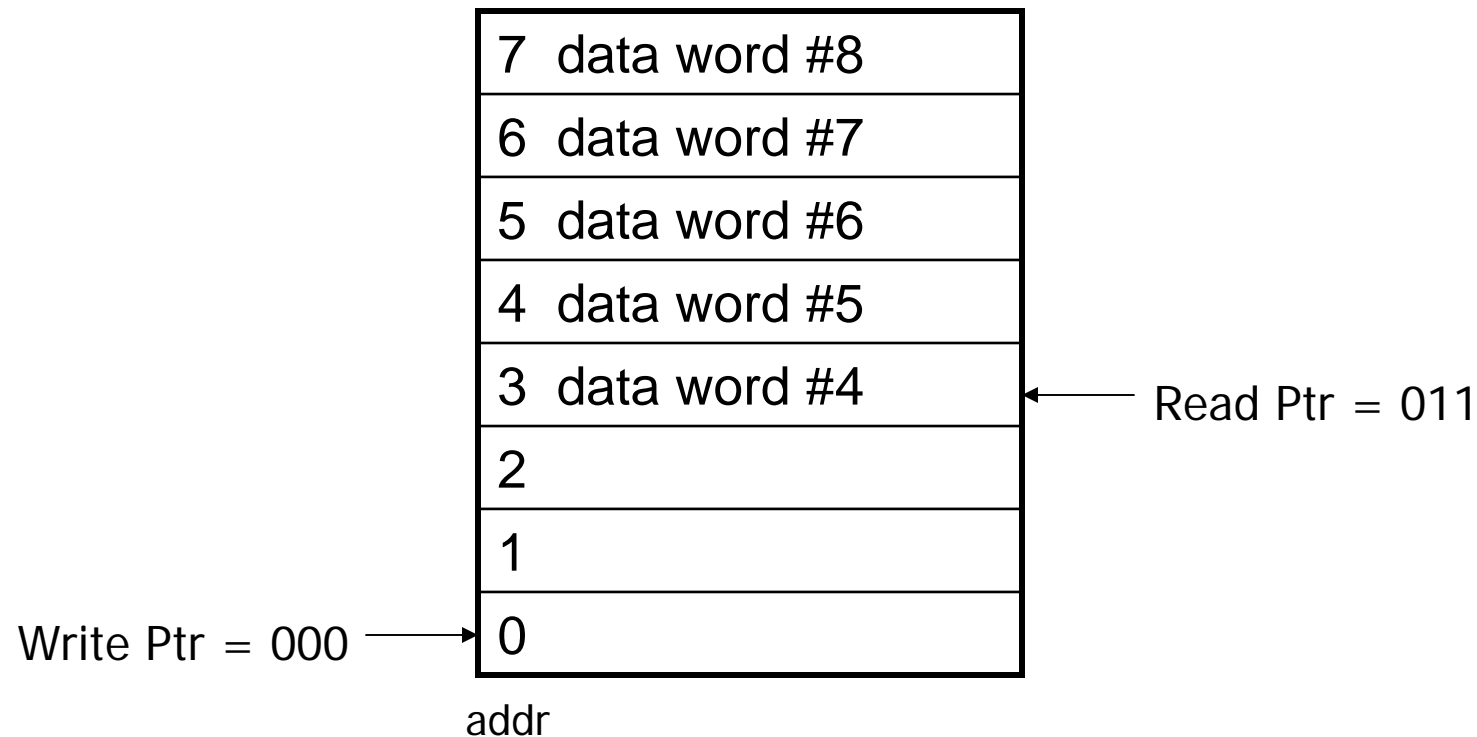

After 2 more words read

# FIFO Implementation

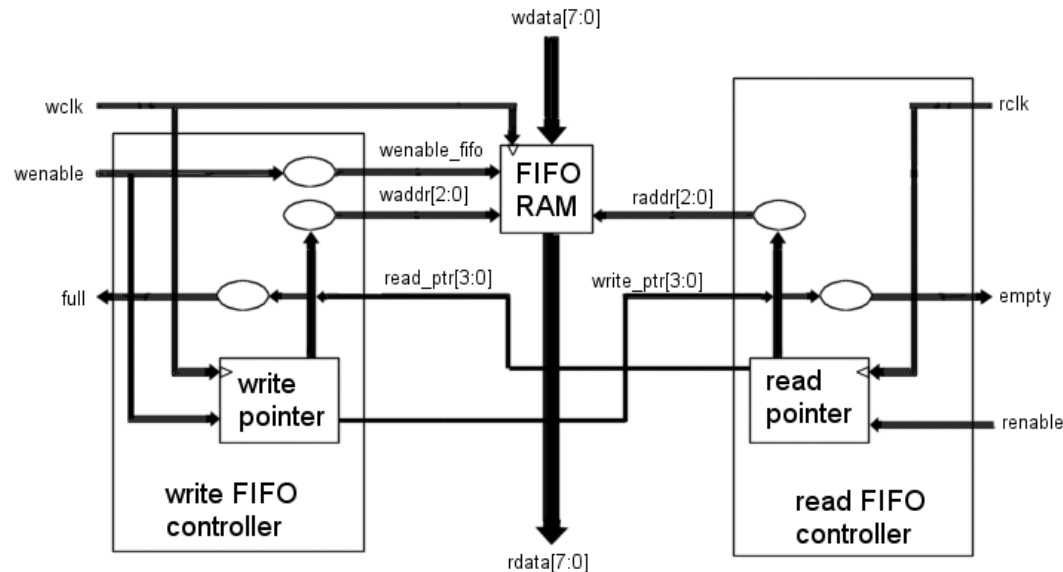

Write controller:  
Checks for full condition.  
If not full, writes data & increments write pointer.

FIFO RAM:  
A set of 8 registers, 8 bits each, with addressing logic

Read controller:  
Checks for empty condition. If not full, increments the read pointer.